
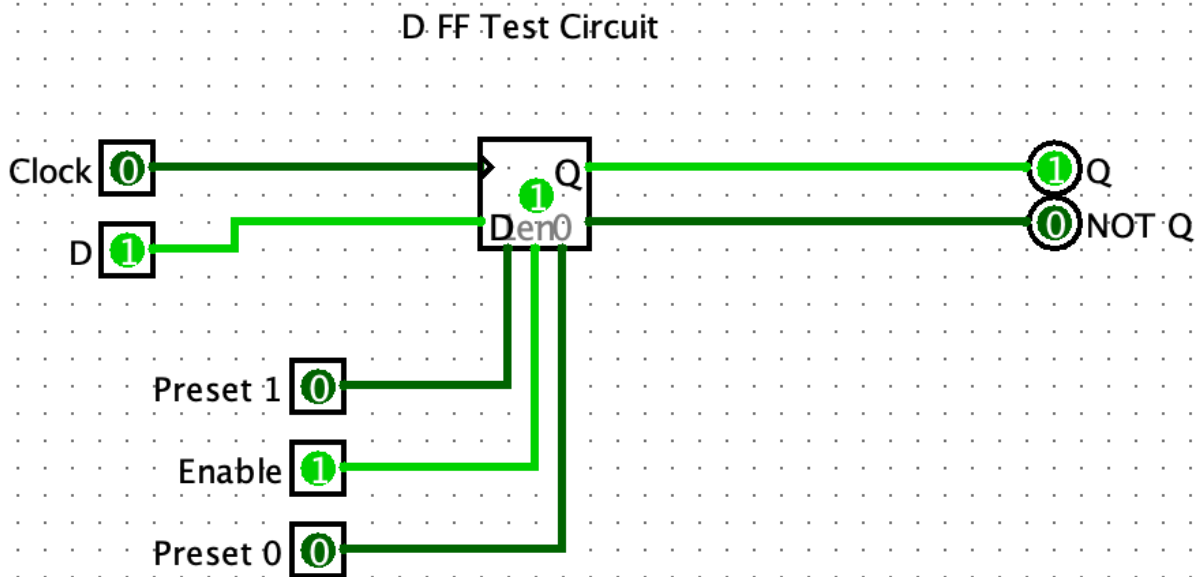


Lab 1
Owen Monus
CS 301
200482797
Jan 13, 2024

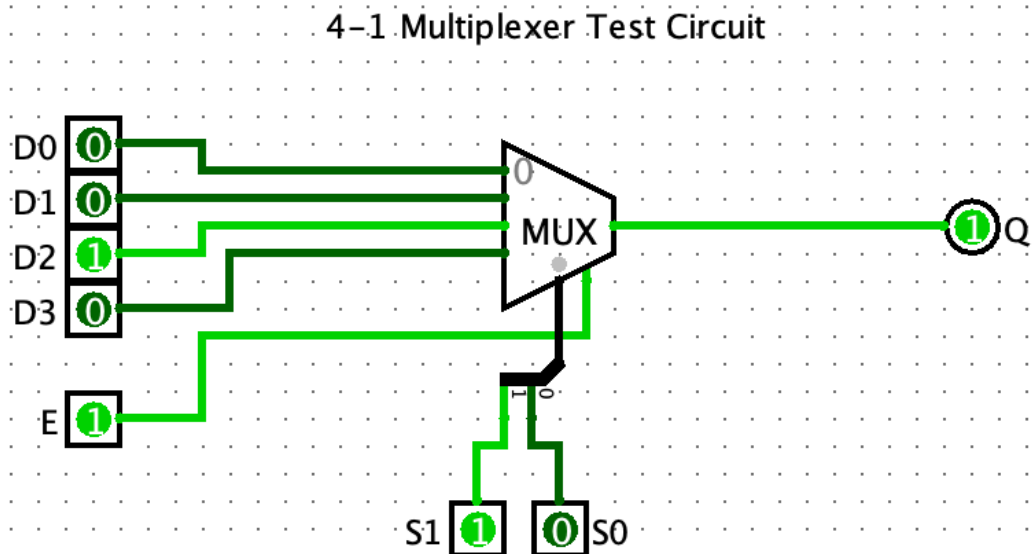
testing circuit of the one bit D-flip-flop




testing circuit of the one bit 4-1 Multiplexer



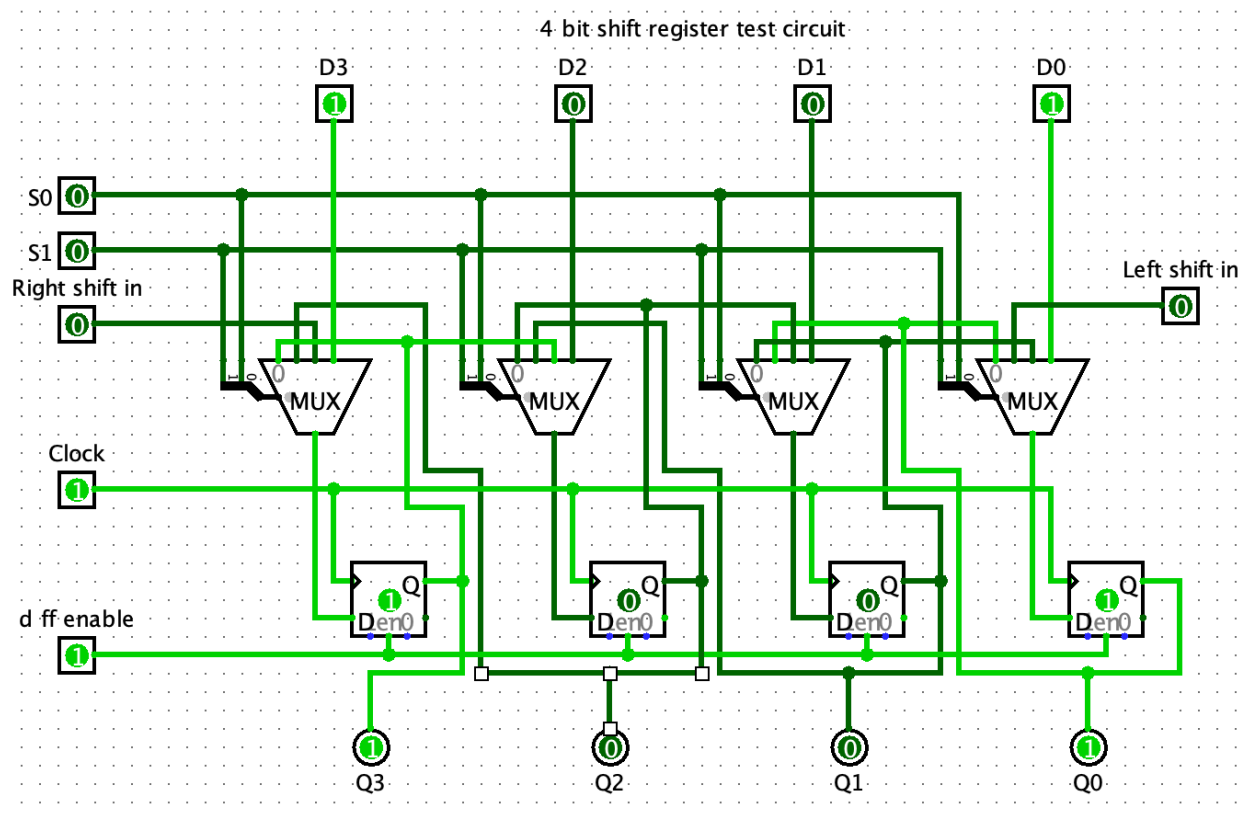
circuit implementing the 4-bit shift register design




Store 0,0

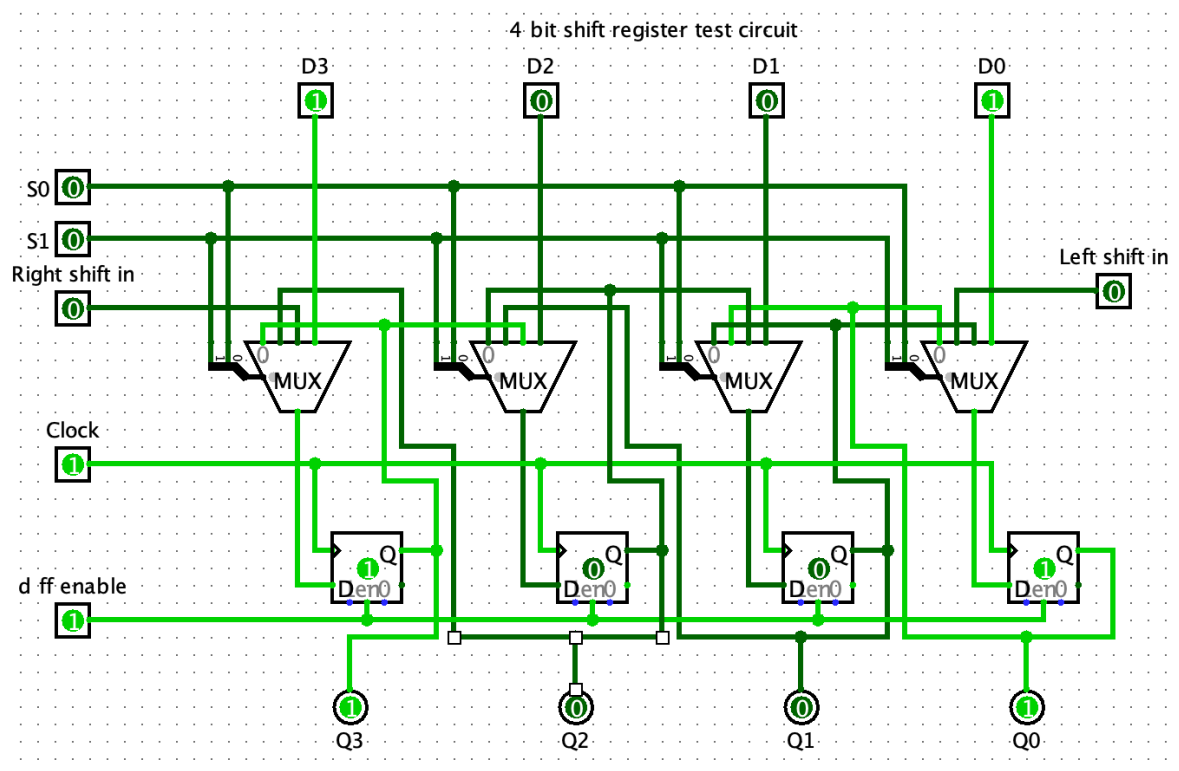

Shift left 0,1

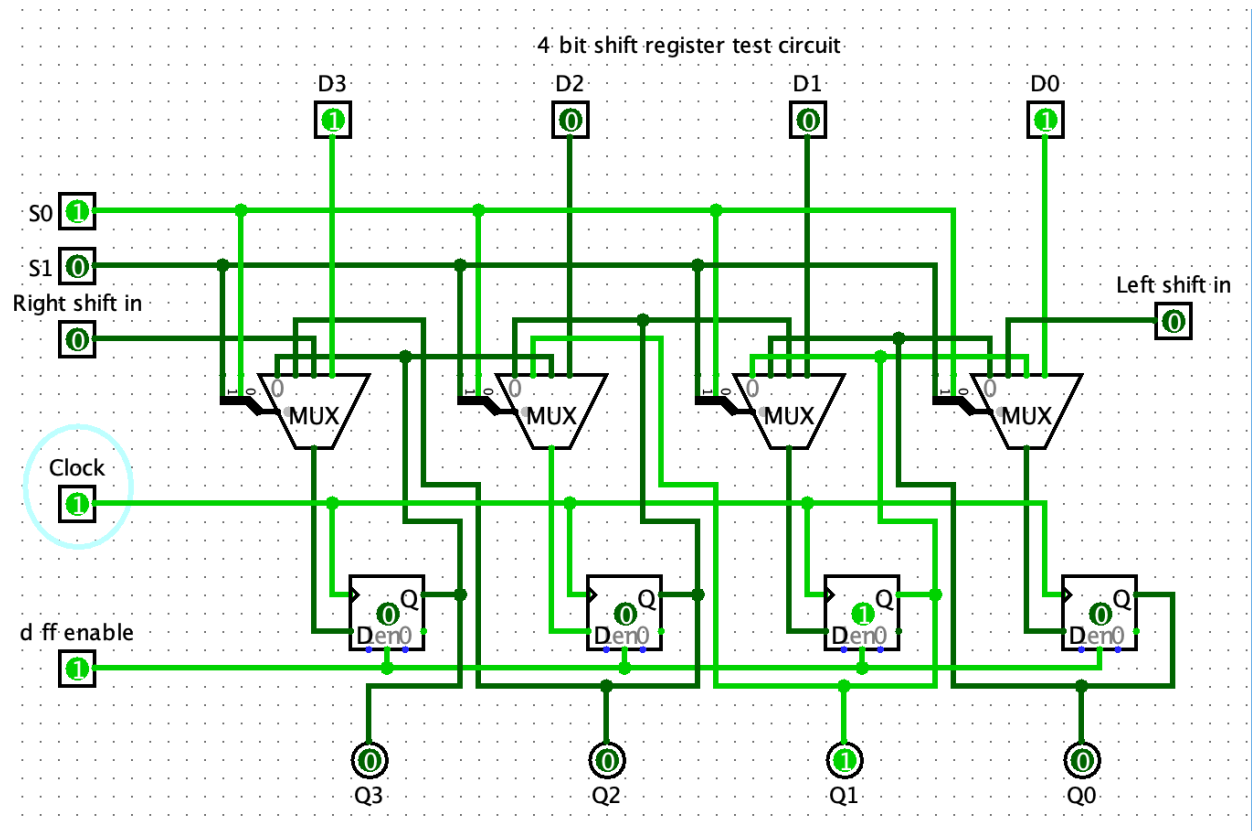

Shift right, 1,0

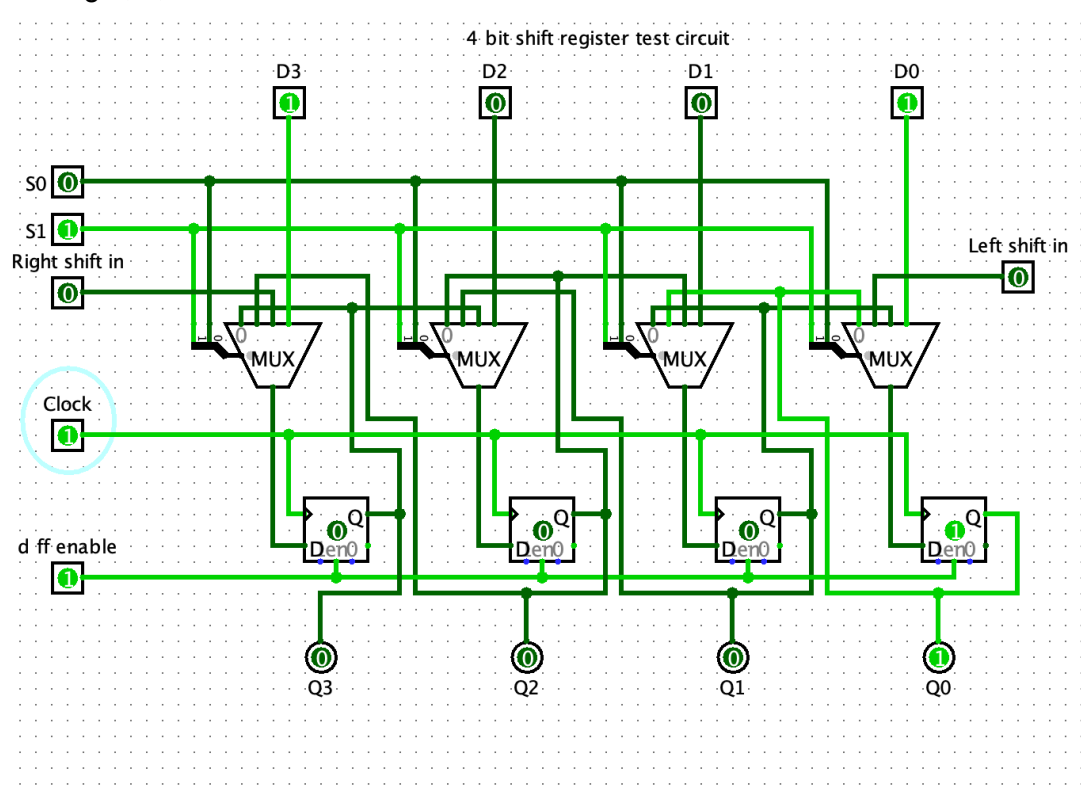

Load 1,1

